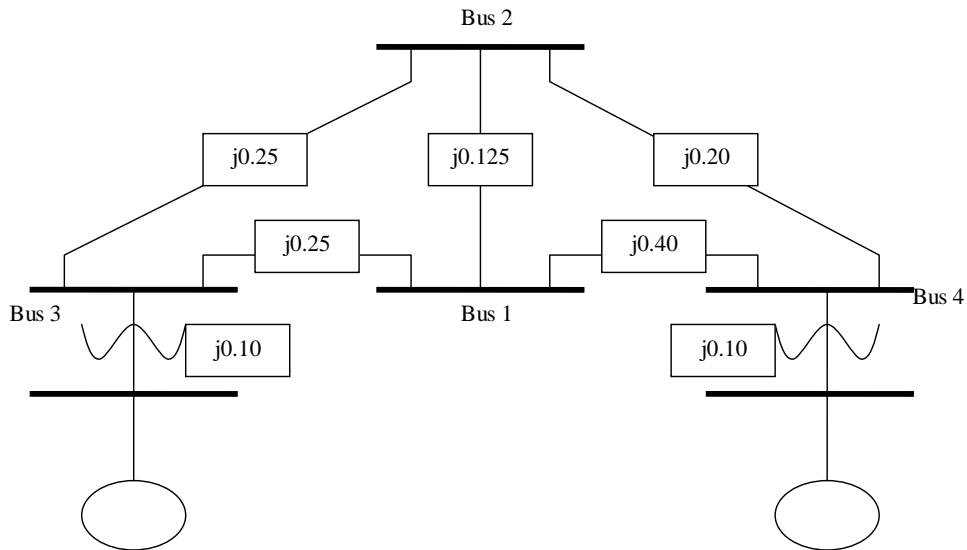


## HW3 Solutions

1. Problem 9.8 (see end of this document)
2. Consider the 4-bus system shown below. Both machines have subtransient reactances of 0.20 pu (you can combine the machine subtransient reactance with the transformer impedance to get a single reactance connecting the machine internal voltage with the network).



- a. Construct the  $Y$ -bus for this network (should be a  $4 \times 4$  matrix).
- b. Consider that there is a three-phase (symmetrical) fault at bus 2.
  - ii. Use LU decomposition to obtain the 2<sup>nd</sup> column of the  $Z$ -bus.
  - iii. Compute the subtransient fault current.
  - iv. Use eq. (12) to find the voltages during the fault.
  - v. Use eq. (17) to find the subtransient currents in lines 3-2, 1-2, and 4-2.

**Solution:**

a). Compute the Y-Bus

$$Y_{bus} = \begin{bmatrix} \frac{1}{j.25} + \frac{1}{j.125} + \frac{1}{j.40} & \frac{-1}{j.125} & \frac{-1}{j.25} & \frac{-1}{j.4} \\ \frac{-1}{j.125} & \frac{1}{j.25} + \frac{1}{j.125} + \frac{1}{j.2} & \frac{-1}{j.25} & \frac{-1}{j.2} \\ \frac{-1}{j.25} & \frac{-1}{j.25} & \frac{1}{j.25} + \frac{1}{j.25} + \frac{1}{j.3} & 0 \\ \frac{-1}{j.4} & \frac{-1}{j.25} & 0 & \frac{1}{j.2} + \frac{1}{j.3} + \frac{1}{j.40} \end{bmatrix}$$

$$Y_{bus} = \begin{bmatrix} -j14.5 & j8 & j4 & j2.5 \\ j8 & -j17 & j4 & j5 \\ j4 & j4 & -j11.3333 & 0 \\ j2.5 & j5 & 0 & -j10.83333 \end{bmatrix}$$

b).

i). LU Decomposition to obtain  $Z_2$

$$Y_{bus} Z_{bus} = I$$

$$Y_{bus} Z_2 = \begin{bmatrix} 0 \\ 1 \\ 0 \\ 0 \end{bmatrix}$$

Factorization of a matrix  $\underline{Y}$  can be done efficiently and easily using the matlab command:

$$[\underline{L}, \underline{U}] = \text{lu}(\underline{Y})$$

Then it is easy to find  $\underline{w}$  by hand using forward substitution from:

$$\underline{L}\underline{w} = \underline{I}_k$$

$$\rightarrow \underline{L}\underline{w} = \begin{bmatrix} 0 \\ 1 \\ 0 \\ 0 \end{bmatrix}$$

And then it is easy to find  $\underline{Z}_2$  by hand using backwards substitution from:

$$\underline{U}\underline{Z}_2 = \underline{w}$$

Alternatively, the manual steps of LU decomposition can be performed per the notes from "LU Decomposition." I did it within Matlab, as follows. Here, y1 is the initial "augmented" matrix (see notes on LU decomposition for the meaning of this term).

```
>> y1=[-14.5i,8i,4i,2.5i,0;8i,-17i,4i,5i,1;4i,4i,-11.33333i,0,0;2.5i,5i,0,-10.833333i,0]
```

```
y1 =
```

```
0 -14.5000i    0 + 8.0000i    0 + 4.0000i    0 + 2.5000i    0
0 + 8.0000i    0 -17.0000i    0 + 4.0000i    0 + 5.0000i    1.0000
0 + 4.0000i    0 + 4.0000i    0 -11.3333i    0              0
0 + 2.5000i    0 + 5.0000i    0              0 -10.8333i    0
```

```
>> y2=[y1(1,:)/y1(1,1);y1(2,:);y1(3,:);y1(4,:)]
```

```
y2 =
```

```
1.0000    -0.5517    -0.2759    -0.1724    0
0 + 8.0000i    0 -17.0000i    0 + 4.0000i    0 + 5.0000i    1.0000
0 + 4.0000i    0 + 4.0000i    0 -11.3333i    0              0
0 + 2.5000i    0 + 5.0000i    0              0 -10.8333i    0
```

```
>> y3=[y2(1,:);y2(1,:)*-y1(2,2)+y2(2,:);y2(1,:)*-y1(3,3)+y2(3,:);y2(1,:)*-y1(4,4)+y2(4,:)]
```

```
y3 =
```

```
1.0000    -0.5517    -0.2759    -0.1724    0
0 +25.0000i    0 -26.3793i    0 - 0.6897i    0 + 2.0690i    1.0000
0 +15.3333i    0 - 2.2529i    0 -14.4598i    0 - 1.9540i    0
0 +13.3333i    0 - 0.9770i    0 - 2.9885i    0 -12.7011i    0
```

```
>> y3=[y2(1,:);y2(1,:)*-y1(2,1)+y2(2,:);y2(1,:)*-y1(3,1)+y2(3,:);y2(1,:)*-y1(4,1)+y2(4,:)]
```

```
y3 =
```

```
1.0000    -0.5517    -0.2759    -0.1724    0
0          0 -12.5862i    0 + 6.2069i    0 + 6.3793i    1.0000
0          0 + 6.2069i    0 -10.2299i    0 + 0.6897i    0
0          0 + 6.3793i    0 + 0.6897i    0 -10.4023i    0
```

```
>> y4=[y3(1,:);y3(2,:)/y3(2,2);y3(3,:);y3(4,:)]
```

```
y4 =
```

```
1.0000    -0.5517    -0.2759    -0.1724    0
0          1.0000    -0.4932    -0.5068    0 + 0.0795i
0          0 + 6.2069i    0 -10.2299i    0 + 0.6897i    0
0          0 + 6.3793i    0 + 0.6897i    0 -10.4023i    0
```

```
>> y5=[y4(1,:);y4(2,:);y4(2,:)*-y3(3,2)+y4(3,:);y4(2,:)*-y3(4,2)+y4(4,:)]
y5 =
```

```
1.0000    -0.5517    -0.2759    -0.1724         0
         0         1.0000    -0.4932    -0.5068    0 + 0.0795i
         0         0         0 - 7.1689i    0 + 3.8356i    0.4932
         0         0         0 + 3.8356i    0 - 7.1689i    0.5068
```

```
>> y6=[y5(1,:);y5(2,:);y5(3,:)/y5(3,3);y5(4,:)]
```

```
y6 =
```

```
1.0000    -0.5517    -0.2759    -0.1724         0
         0         1.0000    -0.4932    -0.5068    0 + 0.0795i
         0         0         1.0000    -0.5350    0 + 0.0688i
         0         0         0 + 3.8356i    0 - 7.1689i    0.5068
```

```
>> y7=[y6(1,:);y6(2,:);y6(3,:);y6(3,:)*-y5(4,3)+y6(4,:)]
```

```
y7 =
```

```
1.0000    -0.5517    -0.2759    -0.1724         0
         0         1.0000    -0.4932    -0.5068    0 + 0.0795i
         0         0         1.0000    -0.5350    0 + 0.0688i
         0         0         0         0 - 5.1168i    0.7707
```

```
>> y8=[y7(1,:);y7(2,:);y7(3,:);y7(4,:)/y7(4,4)]
```

```
y8 =
```

```
1.0000    -0.5517    -0.2759    -0.1724         0
         0         1.0000    -0.4932    -0.5068    0 + 0.0795i
         0         0         1.0000    -0.5350    0 + 0.0688i
         0         0         0         1.0000    0 + 0.1506i
```

```
>> z4=y8(4,5)
```

```
z4 =
```

```
0 + 0.1506i
```

```
>> z3=y8(3,5)-y8(3,4)*z4
```

```
z3 =
```

$$0 + 0.1494i$$

$$\gg z2=y8(2,5)-y8(2,4)*z4-y8(2,3)$$

$$z2 =$$

$$0.4932 + 0.1558i$$

$$\gg z2=y8(2,5)-y8(2,4)*z4-y8(2,3)*z3$$

$$z2 =$$

$$0 + 0.2295i$$

$$\gg z1=y8(1,5)-y8(1,4)*z4-y8(1,3)*z3-y8(1,2)*z2$$

$$z1 =$$

$$0 + 0.1938i$$

>>

$$\gg Z2=[z1;z2;z3;z4]$$

$$Z2 =$$

$$0 + 0.1938i$$

$$0 + 0.2295i$$

$$0 + 0.1494i$$

$$0 + 0.1506i$$

ii). Compute the subtransient fault current.

$$I_f'' = \frac{V_f}{Z_{22}} = \frac{1}{j.2295} = -j4.3573 \text{ pu } \textit{or} \textit{ } 4.3573 \angle -90^\circ \text{ pu}$$

iii). Use eq. (12) to find the voltages during the fault.

$$V_{if} = V_j - \frac{Z_{jk}}{Z_{kk}} V_f$$

$$V_{1f} = V_1 - \frac{Z_{12}}{Z_{22}} V_f = 1 - \frac{j.1938}{j.2295} 1 = .15556 \text{ pu}$$

$$V_{2f} = 0$$

$$V_{3f} = V_3 - \frac{Z_{32}}{Z_{22}} V_f = .34902 pu$$

$$V_{4f} = V_4 - \frac{Z_{42}}{Z_{22}} V_f = .343791 pu$$

iv). Use eq. (17) to find the subtransient currents in lines 3-2, 1-2, and 4-2.

$$I''_{ij} = -V_f \frac{Z_{ik} - Z_{jk}}{Z_b Z_{kk}}$$

$$I''_{32} = -V_f \frac{Z_{32} - Z_{22}}{Z_b Z_{22}} = -1 \frac{j.1494 - j.2295}{(j.25)(j.2295)} = -j1.39608 pu$$

$$I''_{12} = -V_f \frac{Z_{12} - Z_{22}}{Z_b Z_{22}} = -j1.244 pu$$

$$I''_{42} = -V_f \frac{Z_{42} - Z_{22}}{Z_b Z_{22}} = -j1.71895 pu$$

3. A Y-connected load has balanced currents with a-c-b sequence given by

$$I_{abc} = \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 10\angle 0^\circ \\ 10\angle +120^\circ \\ 10\angle -120^\circ \end{bmatrix}$$

Calculate the sequence currents. How does your answer differ from the answer obtained in Example 1 in these notes?

**Solution:**

$$\begin{aligned} \begin{bmatrix} I_a^0 \\ I_a^+ \\ I_a^- \end{bmatrix} &= \underline{A}^{-1} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} \\ &= \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} 10\angle 0^\circ \\ 10\angle 120^\circ \\ 10\angle -120^\circ \end{bmatrix} \\ &= \begin{bmatrix} 0 \\ 0 \\ 10\angle 0^\circ \end{bmatrix} \end{aligned}$$

In this case the quantity that is non-zero is negative sequence component.

4. A feeder provides service to a delta-connected load having the following phase currents:

$$I_{ab} = 208.3 \angle -18.19^\circ$$


$$I_{bc} = 138.89 \angle -151.788^\circ$$

$$I_{ca} = 131.94 \angle 145.84^\circ$$

- a. For the phase currents:
  - i. Are they balanced or unbalanced?
  - ii. What is their sum?
  - iii. Obtain their sequence quantities.
  - iv. What is the 0-sequence quantity?
- b. Obtain the line currents. For these currents:
  - i. Are they balanced or unbalanced?
  - ii. What is their sum?
  - iii. Obtain their sequence quantities.
  - iv. What is the 0-sequence quantity?
- c. Use what you have learned in the parts (a) and (b) to answer the three questions (ii, iv) from part (b) for the following a-b-c quantities:
  - i. Unbalanced currents into a grounded-Y.
  - ii. Unbalanced currents into an ungrounded-Y.
  - iii. Unbalanced line-to-line voltages.

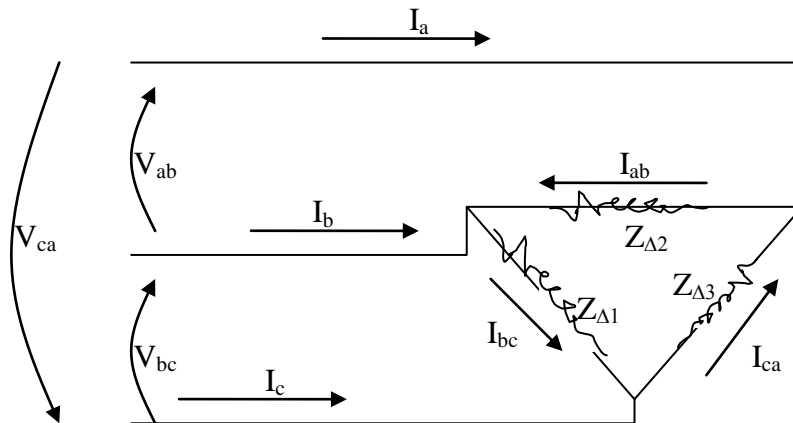**Solution:**

The situation is shown in the figure below.





Part a:

- i. Phase currents are unbalanced.
- ii. Their sum is....

$$I_{ab} + I_{bc} + I_{ca} =$$

$$208.3 \angle -18.19^\circ + 138.89 \angle -151.788^\circ + 131.94^\circ \angle 145.84$$

$$= 65.9252 \angle -121.01^\circ$$

- iii. Their sequence quantities are:

$$\begin{bmatrix} I_{ab}^0 \\ I_{ab}^+ \\ I_{ab}^- \end{bmatrix} = \underline{A}^{-1} \begin{bmatrix} I_{ab} \\ I_{bc} \\ I_{ca} \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} I_{ab} \\ I_{bc} \\ I_{ca} \end{bmatrix}$$

$$= \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} 208.3 \angle -18.19^\circ \\ 138.89 \angle -151.788^\circ \\ 131.94^\circ \angle 145.84 \end{bmatrix}$$

$$= \begin{bmatrix} 21.9531 \angle -120.753^\circ \\ 147.373 \angle -10.5147^\circ \\ 67.0451 \angle -16.699^\circ \end{bmatrix}$$

- iv. The zero-sequence quantity is  $(21.9531 \angle -120.753^\circ)$  (it's non-zero).

Part b: Consider the figure above and note that we may relate the line currents to the phase currents using KCL:

$$I_a = I_{ab} - I_{ca} = (1)I_{ab} + (0)I_{bc} + (-1)I_{ca}$$

$$I_b = -I_{ab} + I_{bc} = (-1)I_{ab} + (1)I_{bc} + (0)I_{ca}$$

$$I_c = -I_{bc} + I_{ca} = (0)I_{ab} + (-1)I_{bc} + (1)I_{ca}$$

Writing in matrix form, we have:

$$I_{abc} = \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 0 & -1 \\ -1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} I_{ab} \\ I_{bc} \\ I_{ca} \end{bmatrix}$$

Denote the matrix as:

$$\underline{K} = \begin{bmatrix} 1 & 0 & -1 \\ -1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix}$$

Now let's use it to obtain the line currents:

$$\begin{aligned} I_{abc} &= \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 0 & -1 \\ -1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} 208.3 \angle -18.19^\circ \\ 138.89 \angle -151.788^\circ \\ 131.94^\circ \angle 145.84 \end{bmatrix} \\ &= \begin{bmatrix} 208.3 \angle -18.19^\circ - 131.94^\circ \angle 145.84 \\ -208.3 \angle -18.19^\circ + 138.89 \angle -151.788^\circ \\ -138.89 \angle -151.788^\circ + 131.94^\circ \angle 145.84 \end{bmatrix} \\ &= \begin{bmatrix} 337.108 \angle -24.3718^\circ \\ 320.282 \angle -179.887^\circ \\ 140.367 \angle 84.5983^\circ \end{bmatrix} \end{aligned}$$

i. They are unbalanced.

ii. Their sum is

$$337.108\angle -24.3718^\circ + 320.282\angle -179.887^\circ + 140.367\angle 84.598^\circ = 0$$

iii. Obtain their sequence quantities.

$$\begin{aligned} \begin{bmatrix} I_a^0 \\ I_a^+ \\ I_a^- \end{bmatrix} &= \underline{A}^{-1} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} \\ &= \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix} \begin{bmatrix} 337.1\angle -24.37^\circ \\ 320.3\angle -168.81^\circ \\ 140.4\angle 84.56^\circ \end{bmatrix} \\ &= \begin{bmatrix} 0 \\ 255.258\angle -40.5147^\circ \\ 116.125\angle 13.301^\circ \end{bmatrix} \end{aligned}$$


iv. The 0-sequence quantity is zero.

Part c:

- i. Unbalanced currents into a grounded-Y will not sum to zero and therefore will have a non-zero zero-sequence component .
- ii. Unbalanced currents into an ungrounded-Y will sum to zero and therefore will have a zero zero-sequence component .
- iii. Unbalanced line-to-line voltages must sum to zero (do a KVL!) and therefore will never have a zero-sequence component.
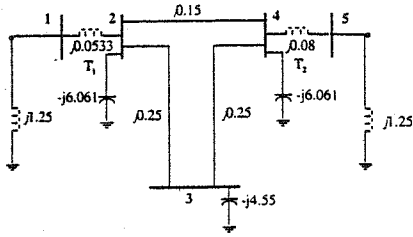
### Problem 9.8

The network considered in Example 9.5 together with the appropriate branch impedances is shown in the figure below



We apply the  $Z_{bus}$  building algorithm described in Section 9.5.

#### Step 1

Add node 1 to the reference node. The branch has a reactance of  $j 1.25$ . This falls under the category Modification 1.

$$Z_{bus} = [j1.25]$$

#### Step 2

Add node 2 to node 1. The branch has a reactance of  $j 0.0533$ . This falls under the category Modification 2.

$$Z_{bus} = \begin{bmatrix} j1.25 & j1.25 \\ j1.25 & j1.3033 \end{bmatrix}$$

#### Step 3

Add node 3 to node 2. The branch has a reactance of  $j 0.25$ . This falls under the category Modification 2.

$$Z_{bus} = \begin{bmatrix} j1.25 & j1.25 & j1.25 \\ j1.25 & j1.3033 & j1.3033 \\ j1.25 & j1.3033 & j1.5533 \end{bmatrix}$$

#### Step 4

Add node 4 to node 3. The branch has a reactance of  $j 0.25$ . This falls under category Modification 2.

$$Z_{bus} = \begin{bmatrix} j1.25 & j1.25 & j1.25 & j1.25 \\ j1.25 & j1.3033 & j1.3033 & j1.3033 \\ j1.25 & j1.3033 & j1.5533 & j1.5533 \\ j1.25 & j1.3033 & j1.5533 & j1.8033 \end{bmatrix}$$

#### Step 5

Add branch between node 2 and node 4. The branch has a reactance of  $j 0.15$ . This falls under category Modification 4.

$$b = \begin{bmatrix} 0 \\ 0 \\ -j0.25 \\ -j0.50 \end{bmatrix} \quad \gamma = (j0.15 + j1.3033 + j1.8033 - (2 \times j1.3033))^{-1} = (j0.65)^{-1} = -j1.5385$$

$$Z_{bus}^n = Z_{bus} - \gamma b b^T$$

$$Z_{bus} = \begin{bmatrix} j1.25 & j1.25 & j1.25 & j1.25 \\ j1.25 & j1.3033 & j1.3033 & j1.3033 \\ j1.25 & j1.3033 & j1.4571 & j1.3610 \\ j1.25 & j1.3033 & j1.3610 & j1.4187 \end{bmatrix}$$

#### Step 6

Add node 5 to node 4. The branch has a reactance of  $j 0.08$ . This falls under the category Modification 2.

$$Z_{bus} = \begin{bmatrix} j1.25 & j1.25 & j1.25 & j1.25 & j1.25 \\ j1.25 & j1.3033 & j1.3033 & j1.3033 & j1.3033 \\ j1.25 & j1.3033 & j1.4571 & j1.3610 & j1.3610 \\ j1.25 & j1.3033 & j1.3610 & j1.4187 & j1.4187 \\ j1.25 & j1.3033 & j1.3610 & j1.4187 & j1.4987 \end{bmatrix}$$

#### Step 7

Add the branch between node 5 and the reference node. The branch has a reactance of  $1.25$ . This falls under the category Modification 3.

We first augment the  $Z_{bus}$  with an additional row and column as shown below

$$Z_{bus} = \begin{bmatrix} j1.25 & j1.25 & j1.25 & j1.25 & j1.25 & j1.25 \\ j1.25 & j1.3033 & j1.3033 & j1.3033 & j1.3033 & j1.3033 \\ j1.25 & j1.3033 & j1.4571 & j1.3610 & j1.3610 & j1.3610 \\ j1.25 & j1.3033 & j1.3610 & j1.4187 & j1.4187 & j1.4187 \\ j1.25 & j1.3033 & j1.3610 & j1.4187 & j1.4987 & j1.4987 \\ j1.25 & j1.3033 & j1.3610 & j1.4187 & j1.4987 & j2.7487 \end{bmatrix}$$

Kron reduce the last row and column to obtain

$$Z_{bus} = \begin{bmatrix} j0.6815 & j0.6573 & j0.6311 & j0.6048 & j0.5685 \\ j0.6573 & j0.6853 & j0.6580 & j0.6306 & j0.5927 \\ j0.6311 & j0.6580 & j0.7832 & j0.6585 & j0.6189 \\ j0.6048 & j0.6306 & j0.6585 & j0.6865 & j0.6452 \\ j0.5685 & j0.5927 & j0.6189 & j0.6452 & j0.6815 \end{bmatrix}$$

We will now add the capacitances due to the half line charging at nodes 2, 3, and 4. This falls under the category Modification 3.

#### Step 8

Add capacitive reactance between node 2 and the reference node. This branch has a reactance of  $(j0.11 + j0.055)^{-1} = -j6.061$

As in step 7 we first augment the original  $Z_{bus}$  with an additional row and column and Kron reduce. The augmented matrix and the Kron reduced matrix are given below.

$$Z_{bus} = \begin{bmatrix} j0.6815 & j0.6573 & j0.6311 & j0.6048 & j0.5685 & j0.6573 \\ j0.6573 & j0.6853 & j0.6580 & j0.6306 & j0.5927 & j0.6853 \\ j0.6311 & j0.6580 & j0.7832 & j0.6585 & j0.6189 & j0.6580 \\ j0.6048 & j0.6306 & j0.6585 & j0.6865 & j0.6452 & j0.6306 \\ j0.5685 & j0.5927 & j0.6189 & j0.6452 & j0.6815 & j0.5927 \\ j0.6573 & j0.6853 & j0.6580 & j0.6306 & j0.5927 & -j5.3757 \end{bmatrix}$$

$$Z_{bus} = \begin{bmatrix} j0.7619 & j0.7411 & j0.7115 & j0.6819 & j0.6409 \\ j0.7411 & j0.7727 & j0.7419 & j0.711 & j0.6683 \\ j0.7115 & j0.7419 & j0.8637 & j0.7357 & j0.6915 \\ j0.6819 & j0.711 & j0.7357 & j0.7604 & j0.7147 \\ j0.6409 & j0.6683 & j0.6915 & j0.7147 & j0.7469 \end{bmatrix}$$

#### Step 9

Add capacitive reactance between node 3 and the reference node. This branch has a reactance of  $(j0.11 + j0.11)^{-1} = -j4.55$

Once again we first augment the original  $Z_{bus}$  and Kron reduce.

$$Z_{bus} = \begin{bmatrix} j0.7619 & j0.7411 & j0.7115 & j0.6819 & j0.6409 & j0.7115 \\ j0.7411 & j0.7727 & j0.7419 & j0.711 & j0.6683 & j0.7419 \\ j0.7115 & j0.7419 & j0.8637 & j0.7357 & j0.6915 & j0.8637 \\ j0.6819 & j0.711 & j0.7357 & j0.7604 & j0.7147 & j0.7357 \\ j0.6409 & j0.6683 & j0.6915 & j0.7147 & j0.7469 & j0.6915 \\ j0.7115 & j0.7419 & j0.8637 & j0.7357 & j0.6915 & -j3.6817 \end{bmatrix}$$

$$Z_{bus} = \begin{bmatrix} j0.8944 & j0.8845 & j0.8785 & j0.821 & j0.7746 \\ j0.8845 & j0.9222 & j0.9159 & j0.8593 & j0.8076 \\ j0.8785 & j0.9159 & j1.0665 & j0.9083 & j0.8537 \\ j0.821 & j0.8593 & j0.9083 & j0.9075 & j0.8529 \\ j0.7746 & j0.8076 & j0.8537 & j0.8529 & j0.8768 \end{bmatrix}$$

#### Step 10

Add capacitive reactance between node 4 and the reference node. This branch has a reactance of

$$(j0.11 + j0.055)^{-1} = -j6.061$$

We again augment the matrix and Kron reduce to obtain

$$Z_{bus} = \begin{bmatrix} j0.8944 & j0.8845 & j0.8785 & j0.821 & j0.7746 & j0.821 \\ j0.8845 & j0.9222 & j0.9159 & j0.8593 & j0.8076 & j0.8593 \\ j0.8785 & j0.9159 & j1.0665 & j0.9083 & j0.8537 & j0.9083 \\ j0.821 & j0.8593 & j0.9083 & j0.9075 & j0.8529 & j0.9075 \\ j0.7746 & j0.8076 & j0.8537 & j0.8529 & j0.8768 & j0.8529 \\ j0.821 & j0.8593 & j0.9083 & j0.9075 & j0.8529 & -j5.1351 \end{bmatrix}$$

$$Z_{bus} = \begin{bmatrix} j1.0312 & j1.0219 & j1.0237 & j0.9693 & j0.911 \\ j1.0219 & j1.0655 & j1.0674 & j1.0106 & j0.9498 \\ j1.0237 & j1.0674 & j1.2266 & j1.0683 & j1.004 \\ j0.9693 & j1.0106 & j1.0683 & j1.0673 & j1.003 \\ j0.911 & j0.9498 & j1.004 & j1.003 & j1.0179 \end{bmatrix}$$